

COMP2611: Computer Organization

Arithmetic Logic Unit

Arithmetic Logic Unit

Review of the 1-bit ALU

- 1-bit ALU
- 1-bit ALU for the MSB
- Overflow detection

An extended 32-bit ALU



- Ripple carry Add/Sub
- SLT implementation

Exercises

A 32-bit ALU can be constructed using the following 1-bit ALUs

❑ 1-bit ALU for bits 0 to 30

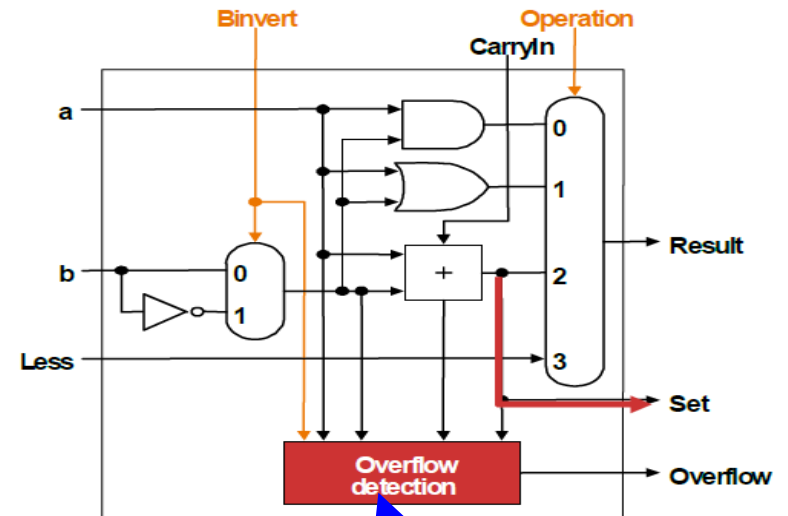 ❑ 1-bit ALU for the Most Significant Bit (MSB): ALU31



Operation	Sign Bit of A	Sign bit of B	Sign bit of Result
A + B	0	0	1
A + B	1	1	0
A - B	0	1	1
A - B	1	0	0

Arithmetic Logic Unit

Review of the 1-bit ALU


- 1-bit ALU
- ALU for the MSB
- Overflow detection

An extended 32-bit ALU

- Ripple carry Add/Sub
- SLT implementation

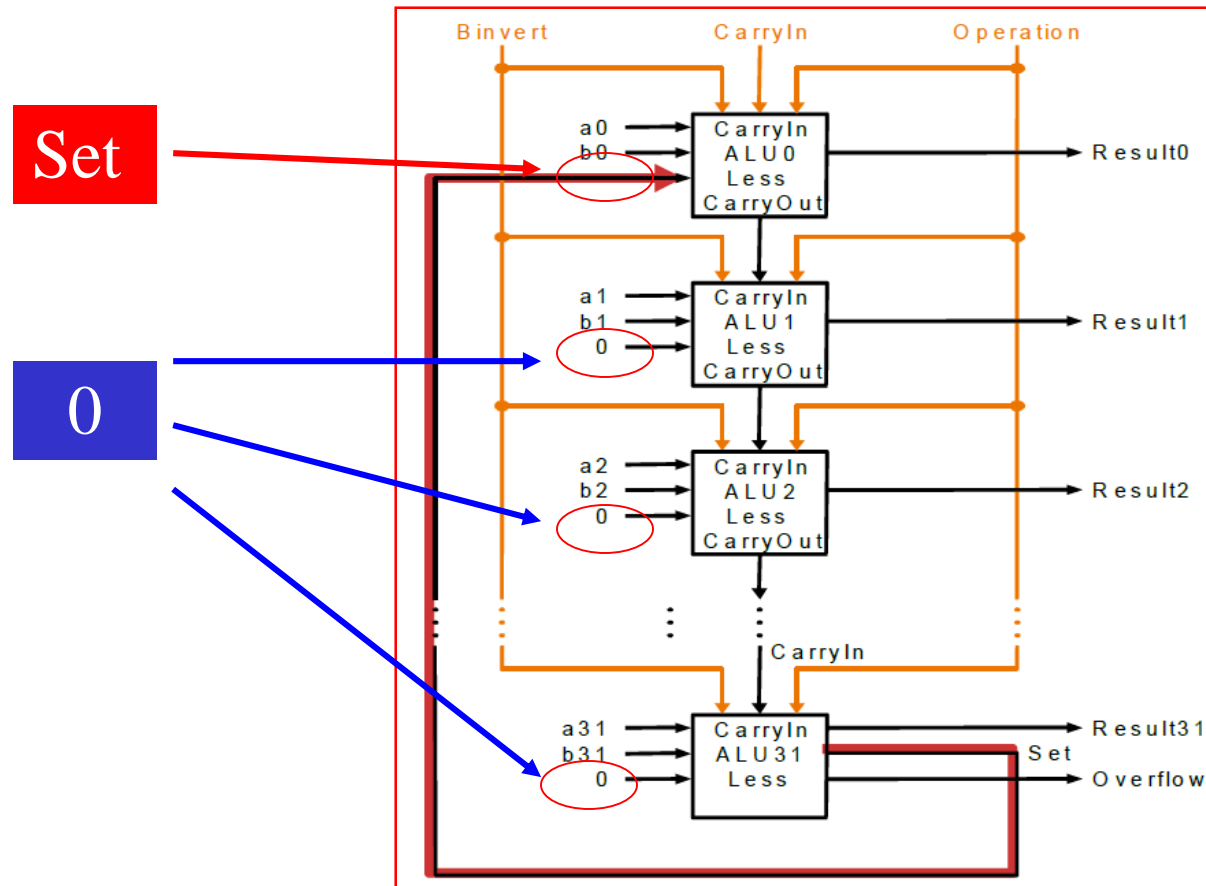Exercises

- ❑ An extended 32-bit ALU (supports SLT) can be formed by connecting 32 1-bit ALUs as follows. Note the 0's at the "Less" input for ALU1-ALU31, note also the **set** signal from ALU31 to ALU0.



Arithmetic Logic Unit

Review of the 1-bit ALU

- 1-bit ALU
- ALU for the MSB
- Overflow detection

An extended 32-bit ALU

- Ripple carry Add/Sub
- SLT implementation

Exercises

Question 1: By referring to slides 3 and 5, explain how SLT operation can be performed. State the values for the control signals **Binvert**, **CarryIn** and **Operation**.

Question 2: By referring to slides 3 and 5, derive the logic expression in the Sum of Product form (SoP) for overflow conditions.

Question 3: The SLT operation depends on the result of $A-B$, and set whenever the sign bit of the operation is asserted. Describe a scenario such that this approach does not work correctly.

Question 5: By referring to the modified 32-bit ALU below, explain how the condition $A==B$ is detected. State the values for the control signals **Bnegate** and **Operation**.

