

# COMP2611: Computer Organization

## Control of the single cycle datapath

- ❑ You will learn the following in this tutorial:
  - ❑ the hardware control units of the single cycle datapath,
  - ❑ the effects of the individual control signals,
  - ❑ how an instruction is executed through the guidance of the control signals.

## Single Cycle Datapath

### Review of the control signals


- the two hardware control units
- the effects of the control signals

### Sample execution of an instruction


- instruction fetch, decoding, executing, memory referencing and writing back
- Exercises
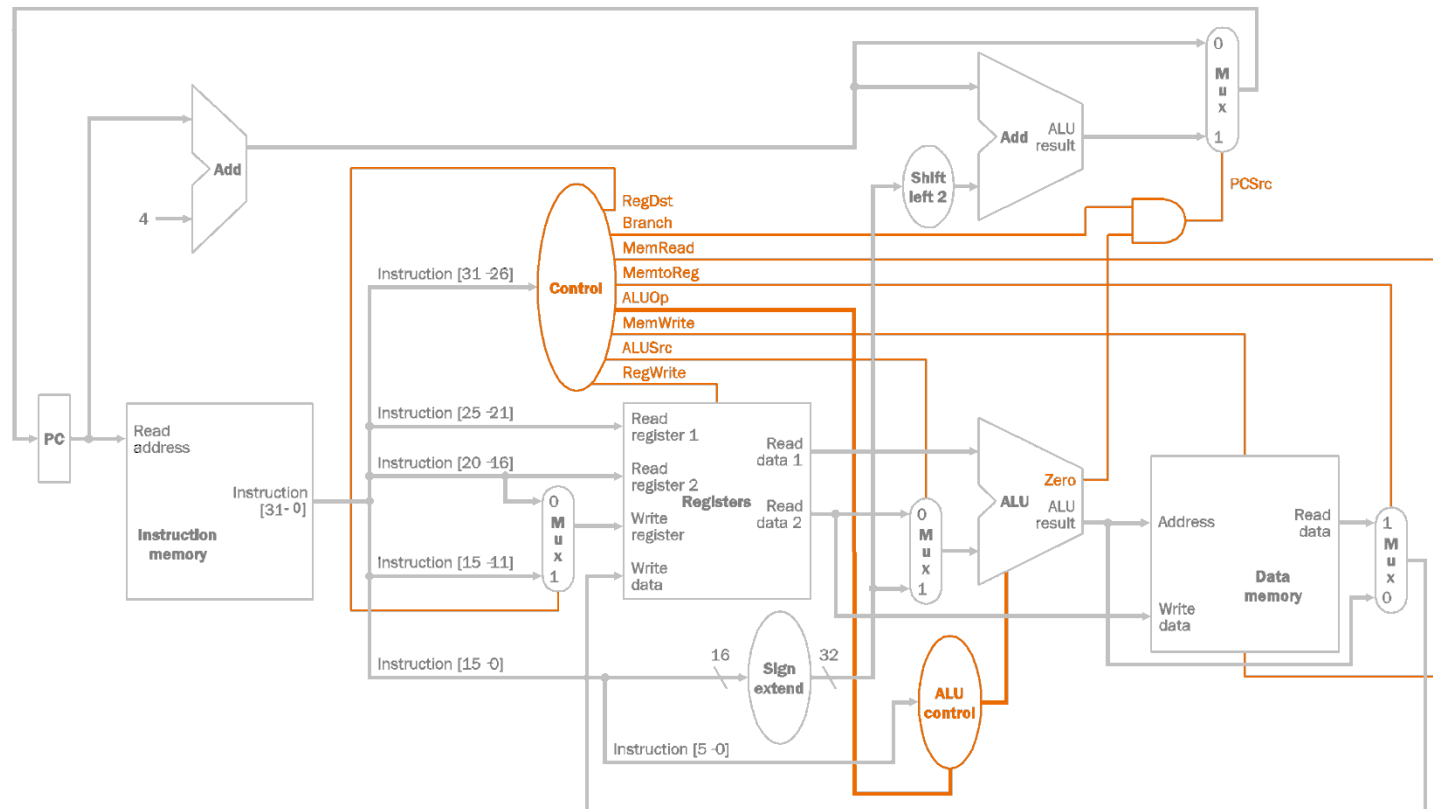
### Exercises

- ❑ The control units of the datapath are responsible for setting all the control signals for the instructions.
- ❑ Two hardware units:
  - ❑ Control – 6 bits of input (bits [31-26]),
  - ❑ ALU Control – 2+6 bits of input (ALUOp from control, bits [5-0])




## 5

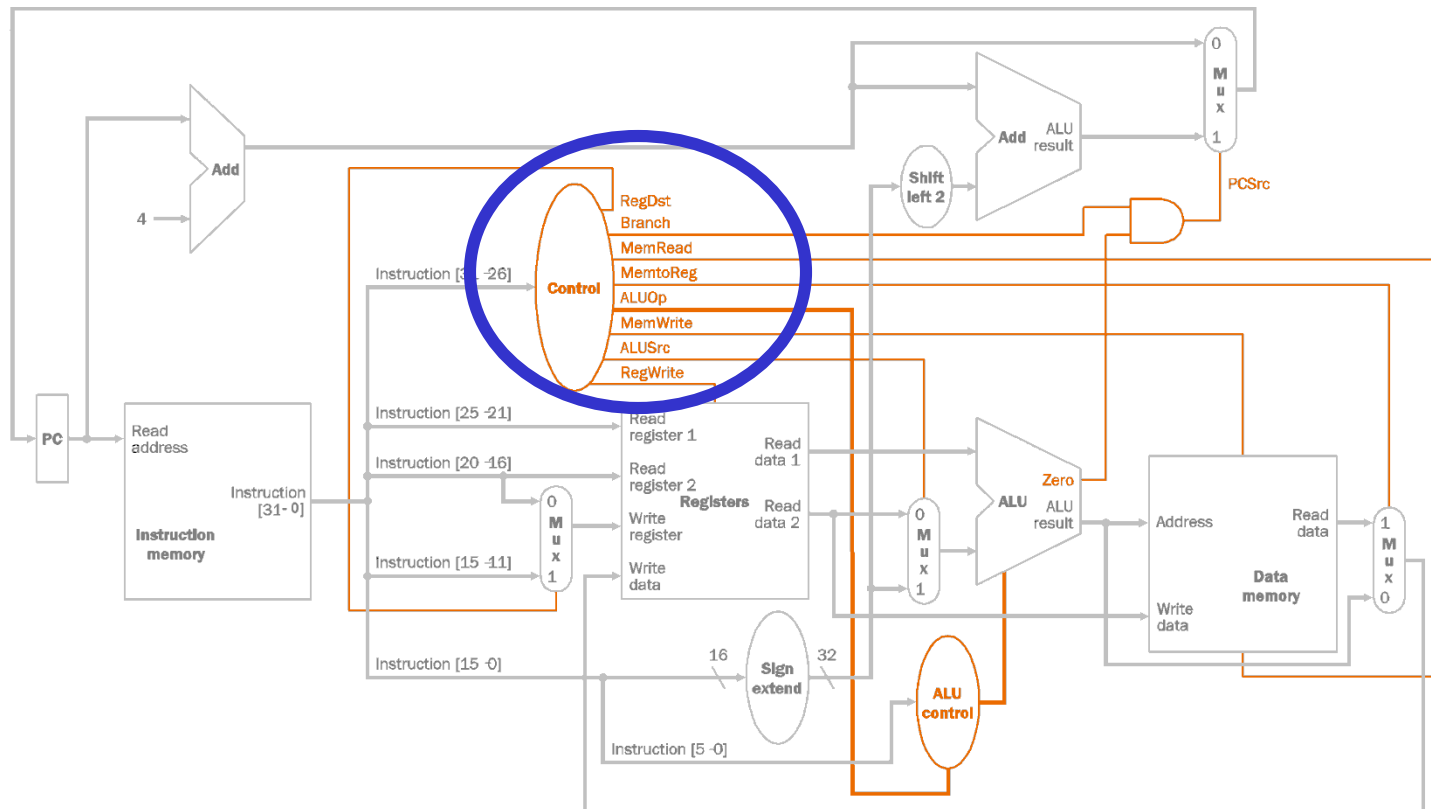

# Review of the Control signals

6

Signal name	Effect when deasserted	Effect when asserted
<b>MemWrite</b>	None	Enable write to the memory. Overwrite the memory contents designated by the address with the value on the write data input
<b>ALUSrc</b>	The Second ALU operand comes from the second register file output (read data port 2)	The second ALU operand is the sign-extended 16-bit data (bits 15-0)
<b>PCSrc</b>	The next PC picks up from the output of the adder that computes PC+4	The next PC picks up the output of from the adder that computes the branch target
<b>RegWrite</b>	None	Enable data write to the register specified by the register destination number

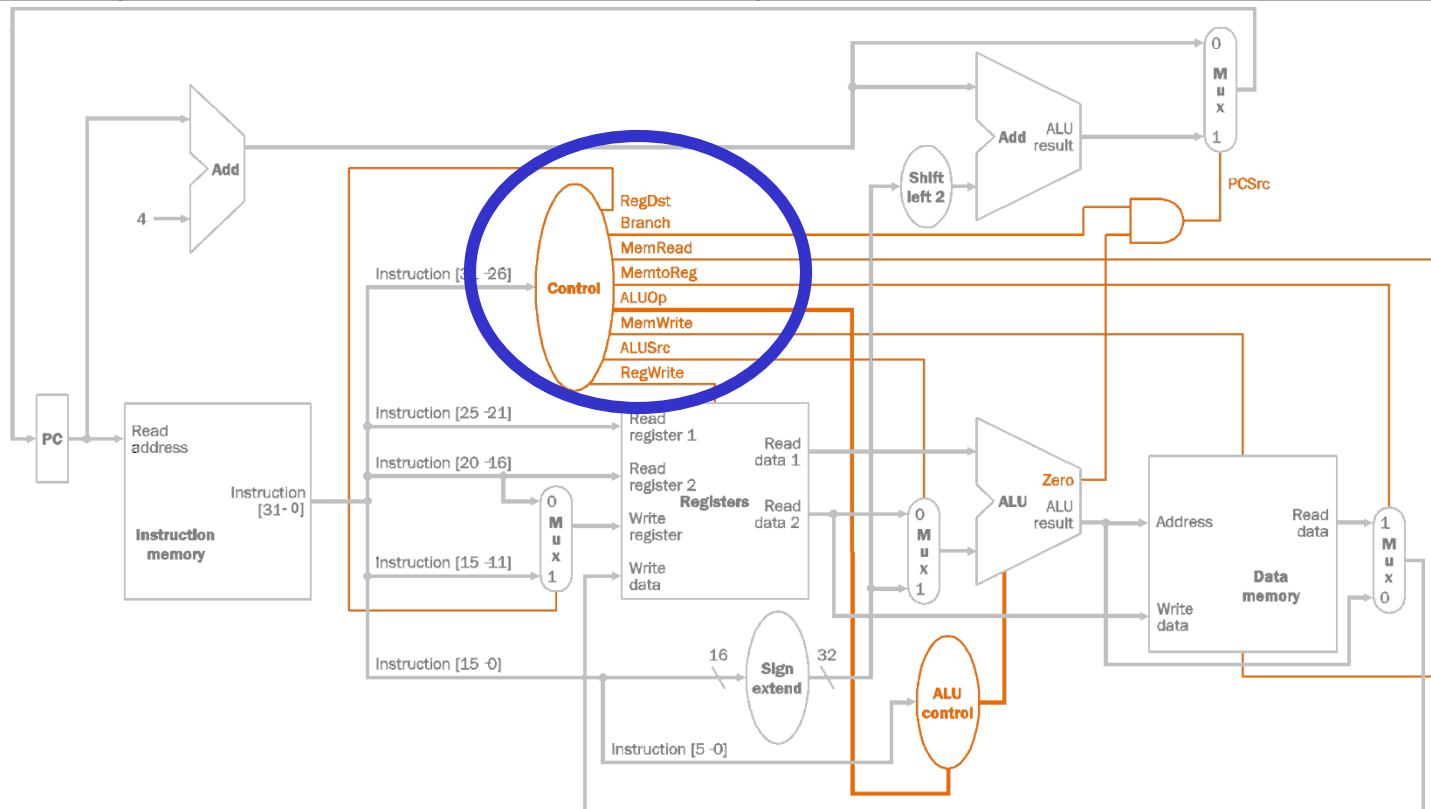


*Control of the single cycle datapath*

# Review of the Control signals

7

ALUOp signal (2-bit)	Effect
00	ADD operation at the ALU for Load/Store instructions
01	SUB operation at the ALU for BEQ
10	ALU operation determined by the funct field (bits 5-0)

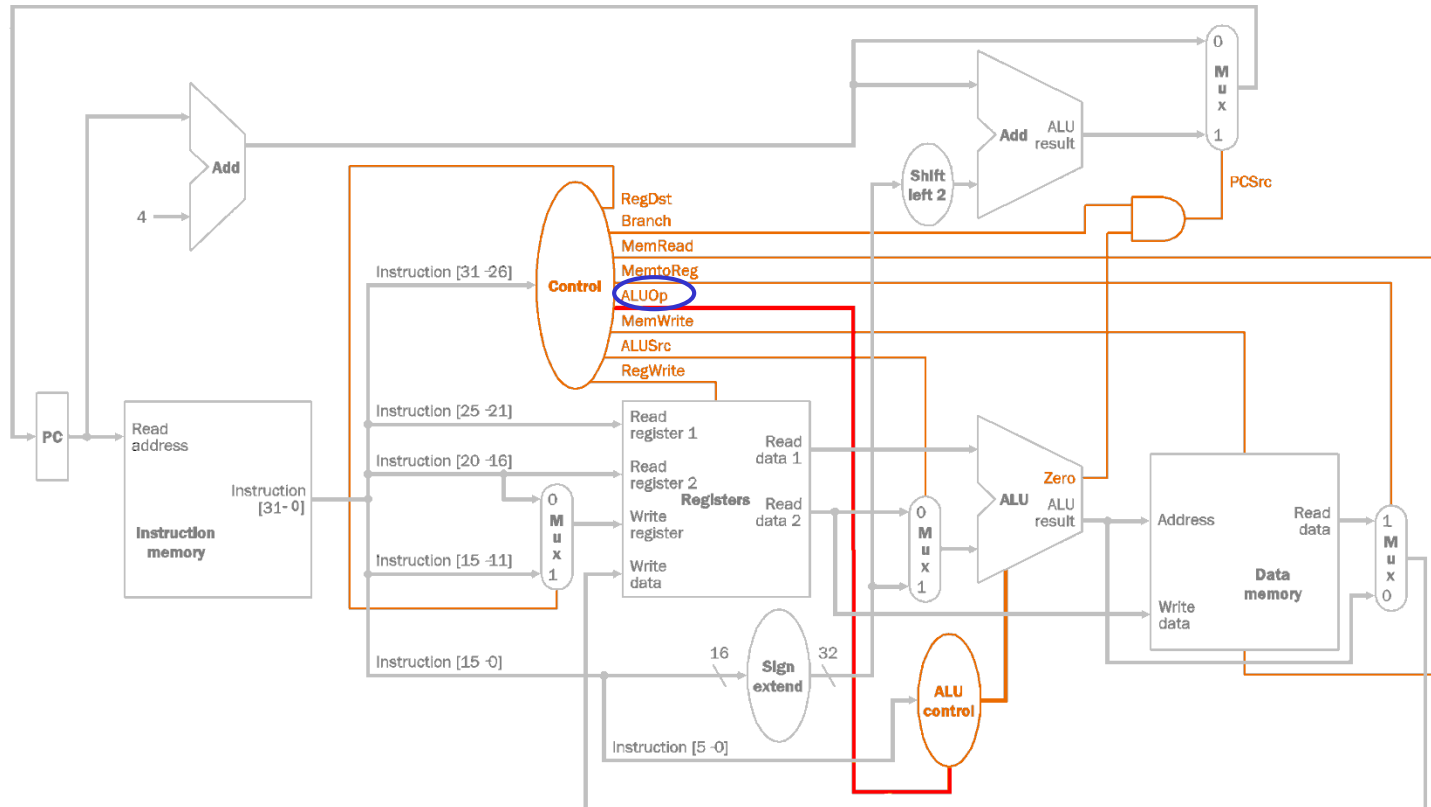


*Control of the single cycle datapath*

# Review of the Control signals

8

ALU control signal (4-bit)	Effect
0000	The ALU will perform the <b>AND</b> operation
0001	The ALU will perform the <b>OR</b> operation
0010	The ALU will perform the <b>ADD</b> operation
0110	The ALU will perform the <b>SUB</b> operation
0111	The ALU will perform the <b>Set on Less Than (SLT)</b> operation
1100	The ALU will perform the <b>NOR</b> operation

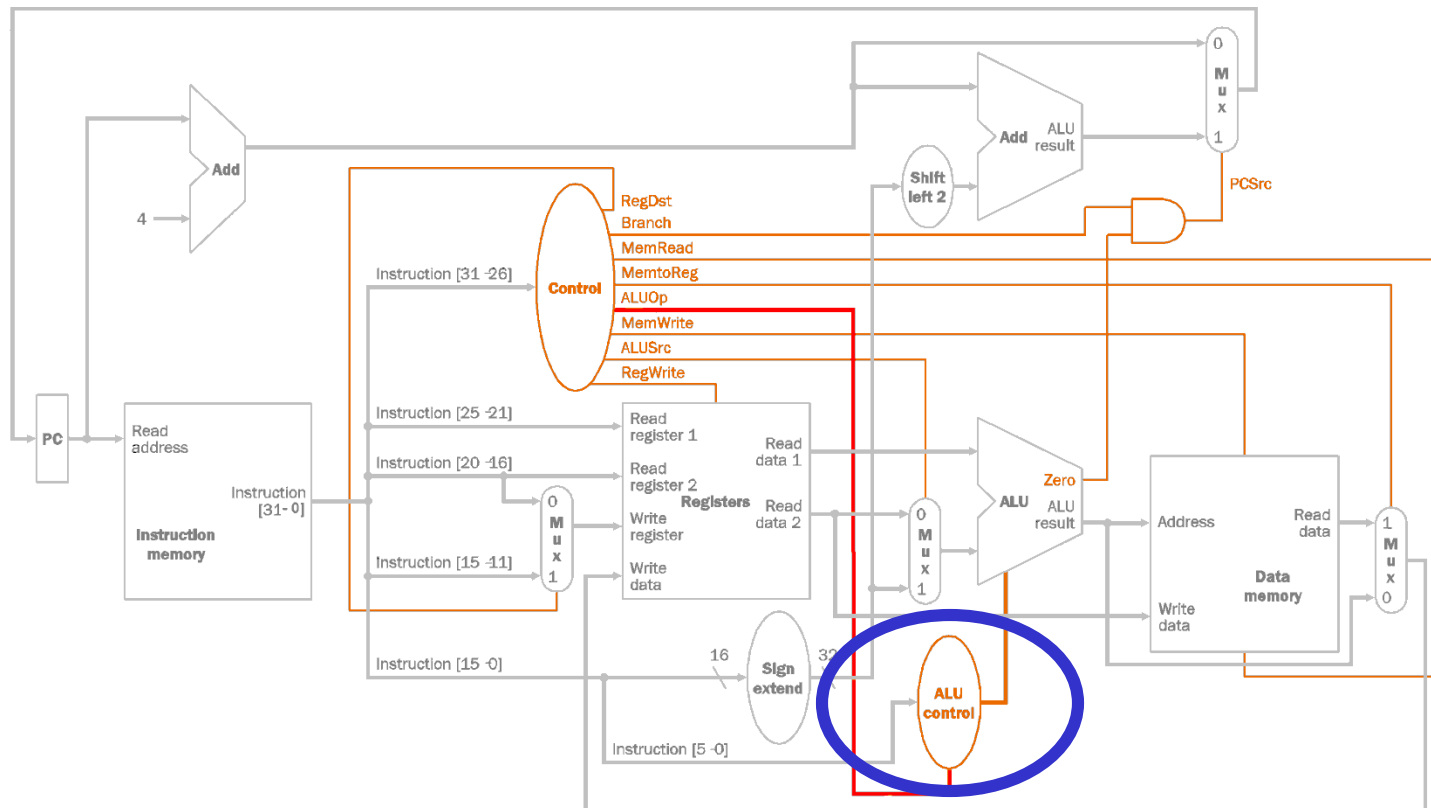

*Control of the single cycle datapath*



## Single Cycle Datapath

Review of the control signals

- the two hardware control units
- the effects of the control signals

Sample execution of an instruction

- instruction fetch, decoding, executing, memory referencing and writing back
- Exercises

Exercises


## ❑ Execution of the R-type instruction "AND"

Description	Bitwise AND operation on the values of the registers Rs and Rt. Store the result in Rd.
Operation	$\$Rd = \$Rs \& \$Rt$ ; $PC = PC + 4$
Syntax	AND $\$Rd, \$Rs, \$Rt$
Encoding	<div>000000 sssss tttt dddd 00000 100100</div> <div>OpCode Rs Rt Rd Shift function</div>

## ❑ Example: AND $\$t0, \$t1, \$t2$

❑ Encoding 000000 01001 01010 01000 00000 100100

## Control signals not yet generated

 

## ❑ Step 2 (decode):


C = 01001, D = 01010, E = 01000

F = value of Rs

G = value of Rt, H = 0000 0000 0000 0000 01000 00000 100100

Instruction fetched:


000000	01001	01010	01000	00000	100100
OpCode	Rs	Rt	Rd	Shift	function

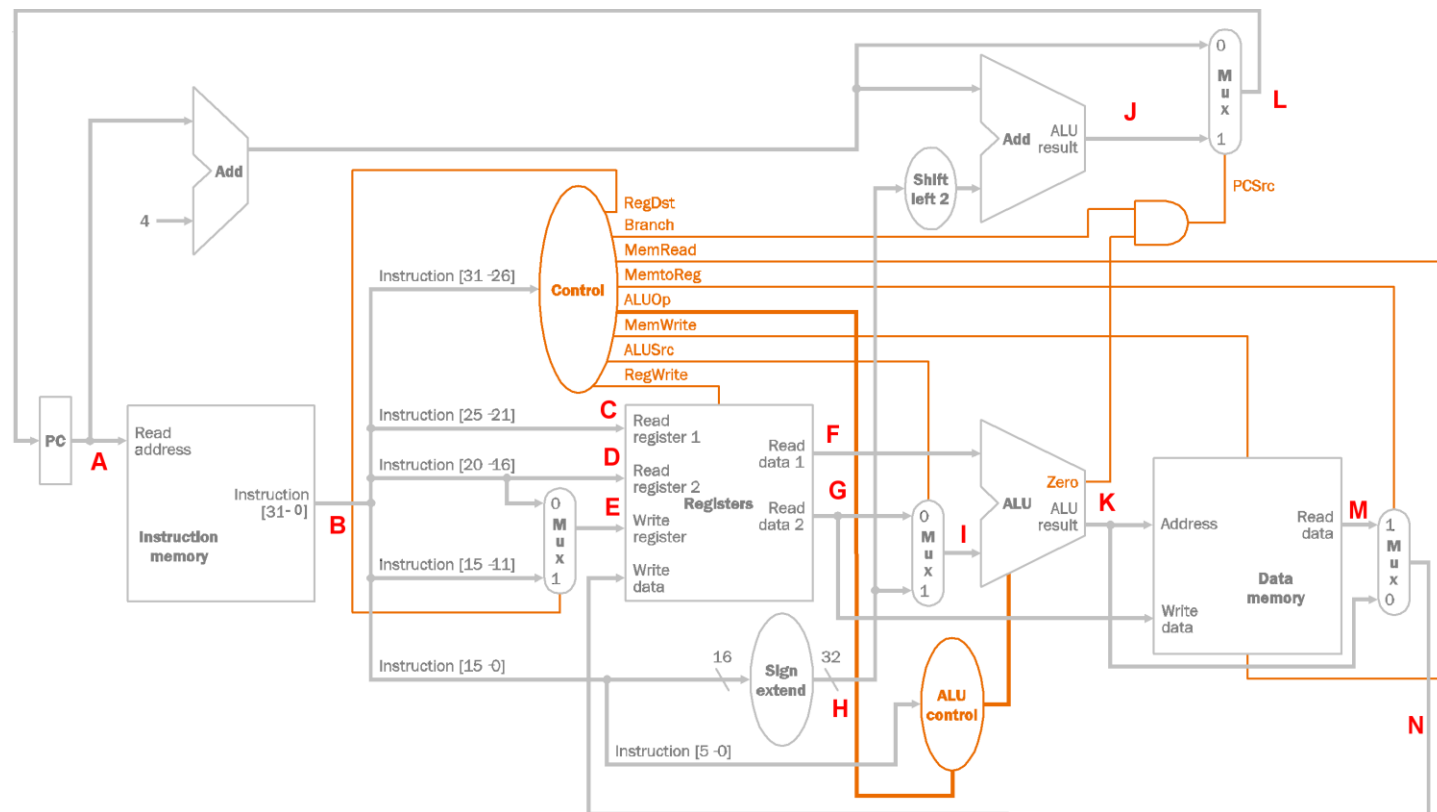
 
## ❑ Step 2 (control signals)

Instruction fetched:

000000 01001 01010 01000 00000 100100  
OpCode Rs Rt Rd Shift function



Control signal	Value
<b>RegDst</b>	1 (R-type instruction)
<b>Branch</b>	0 (not a branch instruction i.e. BEQ)
<b>MemRead</b>	0 (not the LW instruction)
<b>MemtoReg</b>	0 (not the LW instruction)
<b>ALUOp</b>	10 (R-type instruction)
<b>MemWrite</b>	0 (not the SW instruction)
<b>ALUSrc</b>	0 (R-type instruction)
<b>RegWrite</b>	1 (R-type instruction needs to write back)

Inputs		Outputs
Func (bits 5:0)	ALUOp	<b>ALU Control</b>
100 100	10	0000 (AND operation)

## ❑ Step 3 (execution):

**ALUSrc = 0**, therefore I = value of Rt


J = 0000 0000 0000 0001 0000 0000 1001 0000 + PC + 4

**ALU Control = 0000**, therefore K = (value of Rs) bitwise\_AND (value of Rt),

**Branch = 0** => **PCSrc=0**, therefore L = PC+4

Instruction fetched:

000000 01001 01010 01000 00000 100100

 


Instruction fetched:

000000 01001 01010 01000 00000 100100
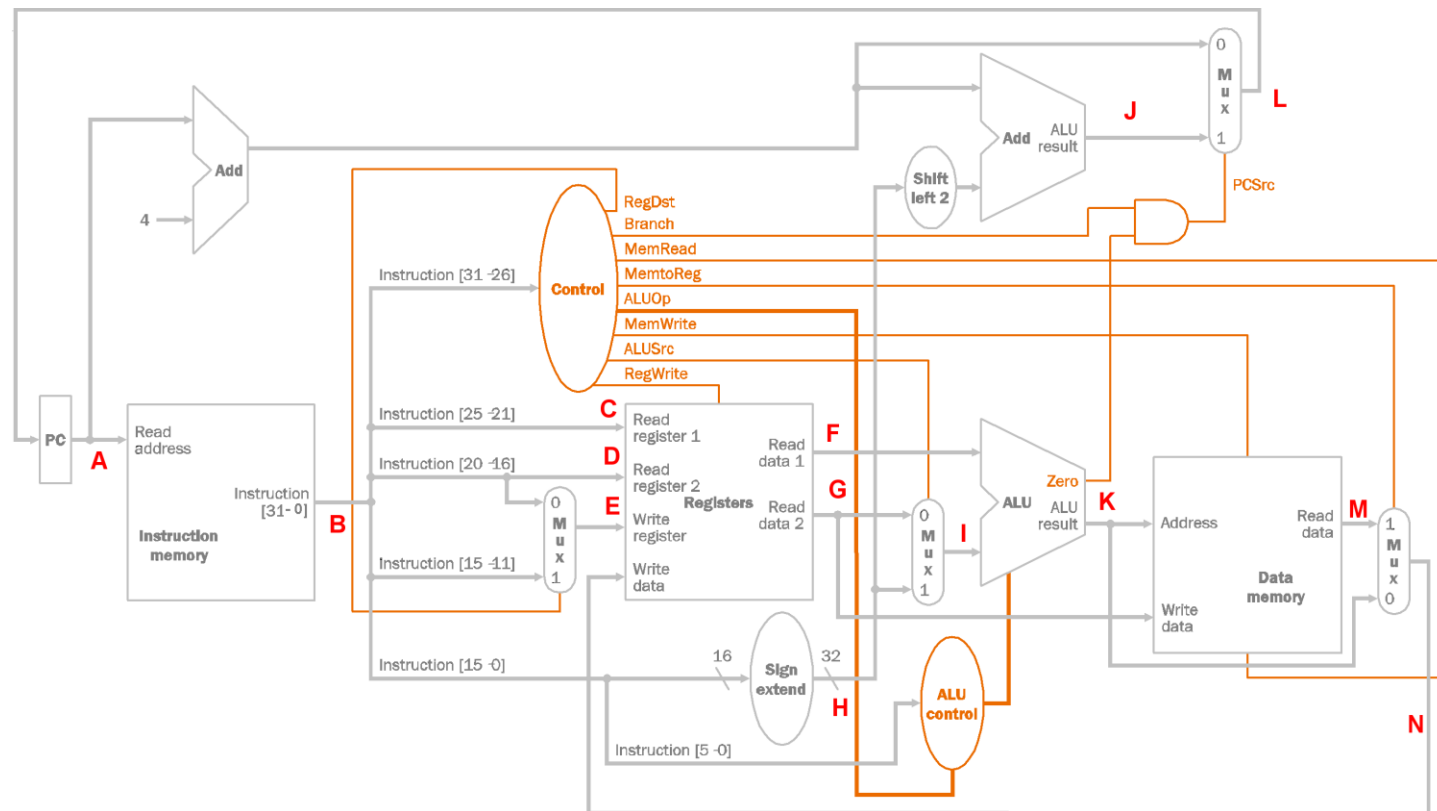
## ❑ Step 4 (memory)

**MemRead=0**, therefore M = Empty (can't read)



## Control of the single cycle datapath

## ❑ Step 5 (write back):


Instruction fetched:

000000 01001 01010 01000 00000 100100

**MemtoReg=0**, therefore N= Results of the ALU

= (value of Rs) bitwise\_AND (value of Rt)

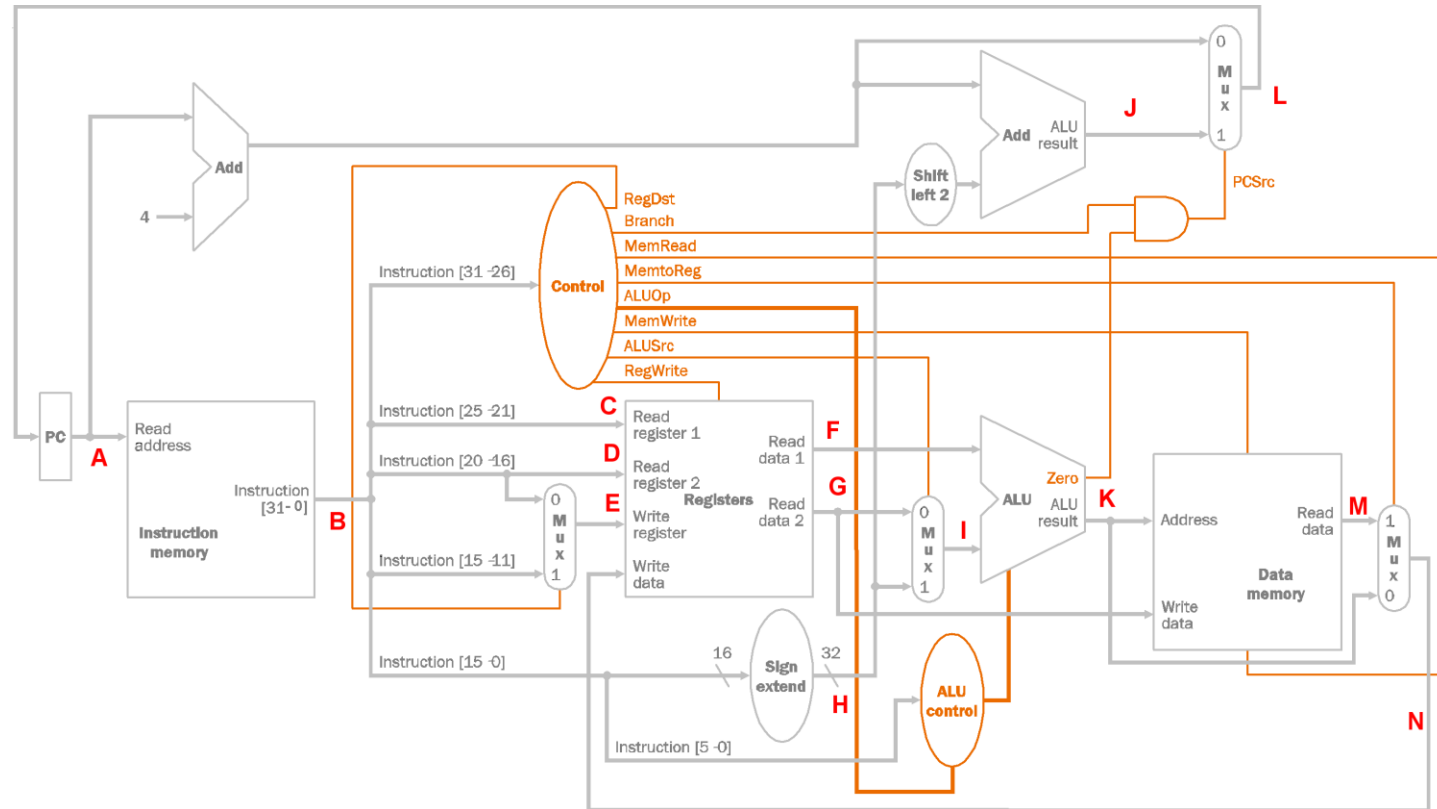**RegWrite=1, RegDst=1**, therefore N is written back to register 01000 (\$t0)





## Single Cycle Datapath

Review of the control signals


- the two hardware control units
- the effects of the control signals

Sample execution of an instruction

- instruction fetch, decoding, executing, memory referencing and writing back
- Exercises

Exercises

**Question 1:** Repeat the execution of the I-type instruction “LW \$t0, 8(\$t1)” by filling the values for A-N and also the control signals.

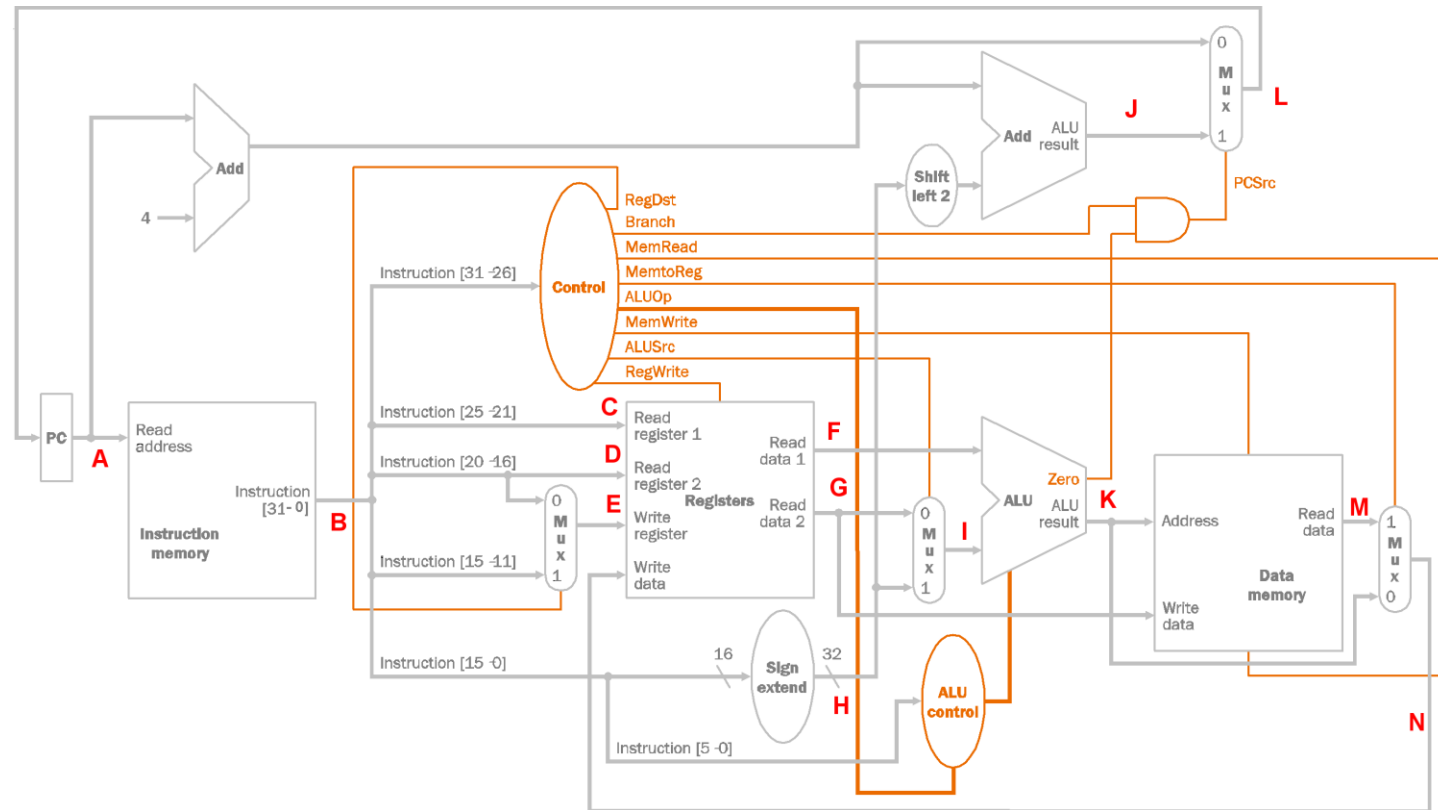

**Question 1:** Repeat the execution of the I-type instruction “LW \$t0, 8(\$t1)” by filling the values for A-N and also the control signals.

**Solution:**

lw \$t0, 8(\$t1) = 100011 01001 01000 0000 0000 0000 1000

Step 1

A = address of the instruction

B = 100011 01001 01000 0000 0000 0000 1000

Step 2

C = 01001, D = 01000, E = 01000, F = value of \$t1, G = value of \$t0

H = 0000 0000 0000 0000 0000 0000 0000 1000

Controls: RegDst=0, Branch=0, MemRead=1, MemtoReg=1, ALUOp=00, MemWrite=0, ALUSrc=1, RegWrite=1, ALU Control=0010

# Exercises

Step 3

$I = 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 1000$

$J = 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0010\ 0000 + PC + 4$

$K = \text{value of } \$t1 + 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 1000, L = PC + 4$


Step 4

$M = \text{mem}[\text{value of } \$t1 + 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 1000]$

Step 5

$N = \text{mem}[\text{value of } \$t1 + 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 1000]$

**Question 2:** Repeat the execution of the I-type instruction "BEQ \$t0, \$t1, 100" by filling the values for A-N and also the control signals. Assume \$t0==\$t1.

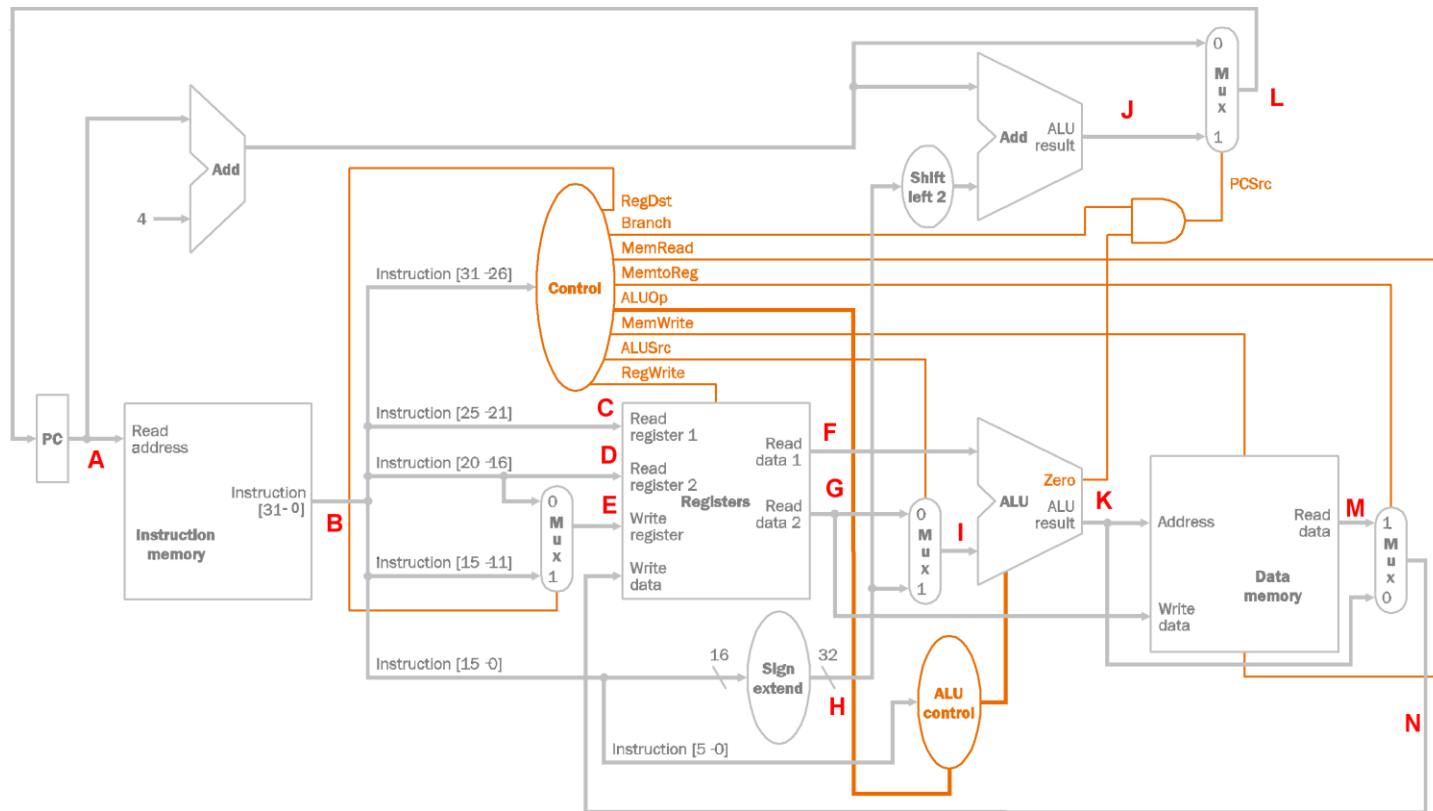

**Question 2:** Repeat the execution of the I-type instruction "BEQ \$t0, \$t1, 100" by filling the values for A-N and also the control signals. Assume \$t0==\$t1.

**Solution:**

beq \$t0, \$t1, 100 = 000100 01000 01001 0000 0000 0110 0100

Step1

A = address of the instruction

B = 000100 01000 01001 0000 0000 0110 0100

Step2

C = 01000, D = 01001, E = either 01001 or 00000, F = value of \$t0, G = value of \$t1

H = 0000 0000 0000 0000 0000 0000 0110 0100

Controls: RegDst=X, Branch=1, MemRead=0, MemtoReg=X, ALUop=01, MemWrite=0, ALUSrc=0, RegWrite=0, ALU Control=0110

# Exercises

Step3

I=value of \$t1

J= 00 0000 0000 0000 0000 0000 0110 010000+PC+4

K=0

Zero=1 (because \$t0==\$t1)

L= 00 0000 0000 0000 0000 0000 0110 010000+PC+4 (because branch=1 and Zero=1)

Step4

M=Empty (can't read)

Step5

MemtoReg=X, so N can't be determined

## Single Cycle Datapath

Review of the control signals

- the two hardware control units
- the effects of the control signals

Sample execution of an instruction

- instruction fetch, decoding, executing, memory referencing and writing back
- Exercises

Exercises



**Question 1:** Repeat the execution of the following instructions by filling the values for A-N and also the control signals :

1) SW    \$t0, 8(\$t1)

2) ADD   \$t0, \$t1, \$t2

3) OR    \$t0, \$t1, \$t2

**Question 2:** Modify the datapath on slide 11 to support the execution of an I-type instruction "LUI \$t0, 100". The instruction shifts the immediate value by 16 bits to the left (lower 16 bits are filled with zeroes) and stores the shifted value to the register. Include all the control signals.

(encoding 000111 00000 tttt iiiiiiiiiiiiiii, t: destination register, i:immediate).

- ❑ Today we have reviewed:
  - ❑ the control units of the single cycle datapath,
  - ❑ the effects of the individual control signals,
  - ❑ how an instruction is executed through the guidance of the control signals.