

COMP2611: Computer Organization

The Processor: Datapath & Control


- ❑ To present the design of MIPS processor
 - **Single-cycle implementation for this class**
- ❑ To illustrate to datapath & control

- ❑ Focus on implementing of a subset of the core MIPS instruction set
 - **Memory-reference instructions:** `lw`, `sw`
 - **Arithmetic-logical instructions:** `add`, `sub`, `and`, `or`, `slt`
 - **Branch and jump instructions:** `beq`, `j`

- ❑ Instructions not included:
 - Integer instructions such as those for multiplication and division
 - Floating-point instructions

- ❑ First, understand how an instruction is executed before the design
- ❑ Next, split the execution of an instruction into multiple steps common to all instructions
- ❑ Next, implement each part separately
- ❑ Finally, put all these parts back together


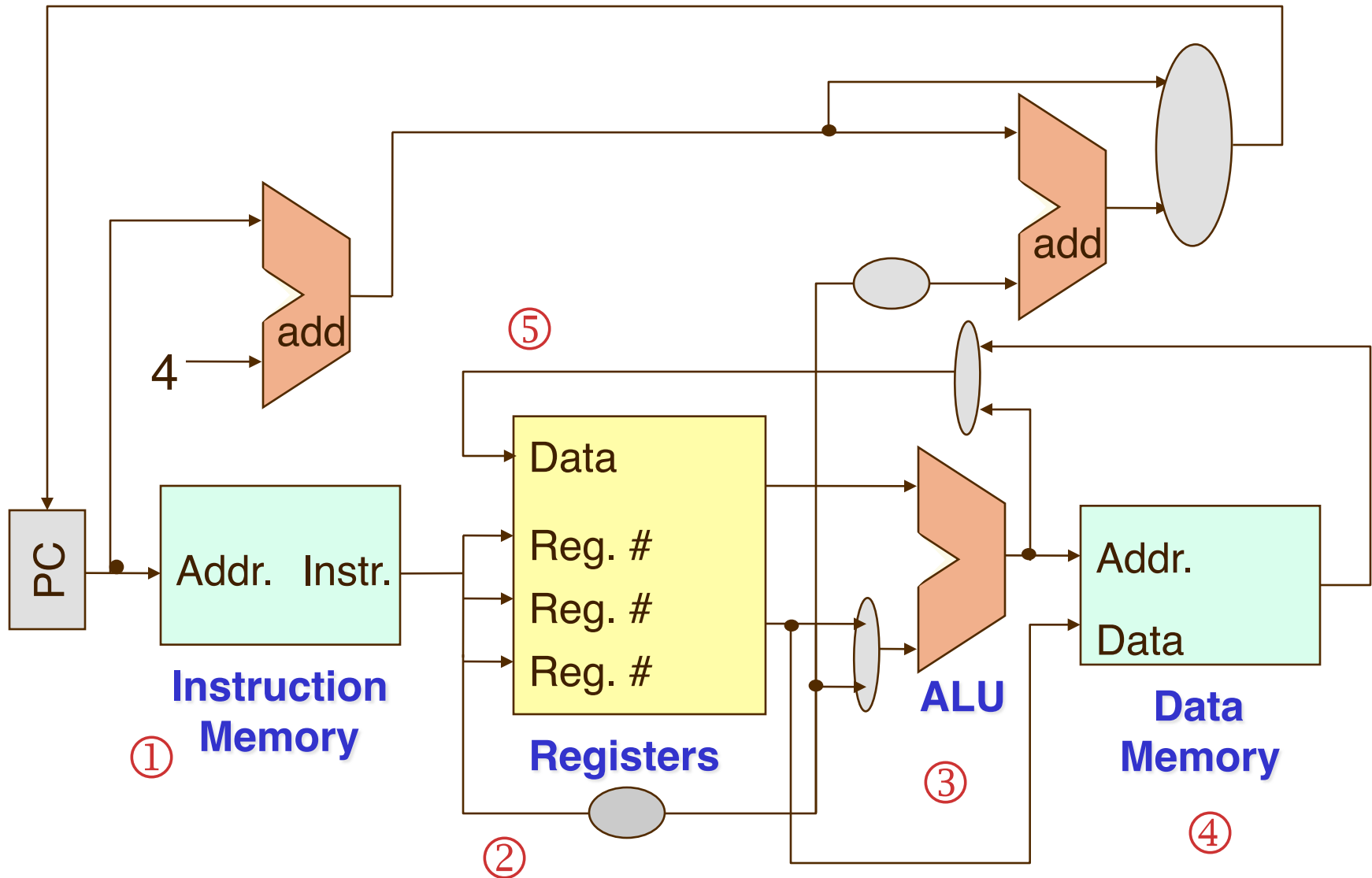
1. **Fetch the instruction** from memory location indicated by program counter (PC)
2. **Decode the instruction** – to find out what to perform
Meanwhile, read source registers specified in the instruction fields
 - **lw** instruction require reading only one register
 - most other instructions require reading **two** registers
3. **Perform the operation** required by the instruction using the ALU
 - Arithmetic & logical instructions: execute
 - Memory-reference instructions: use ALU for address calculation
 - Conditional branch instructions: use ALU for comparison
4. **Memory access**: **lw** and **sw** instructions
5. **Write back the result** to the destination register
Increment PC by 4 or change PC to branch target address



Anatomy of a Computer: Inside the Processor

7

- ❑ AMD Barcelona: 4 processor cores

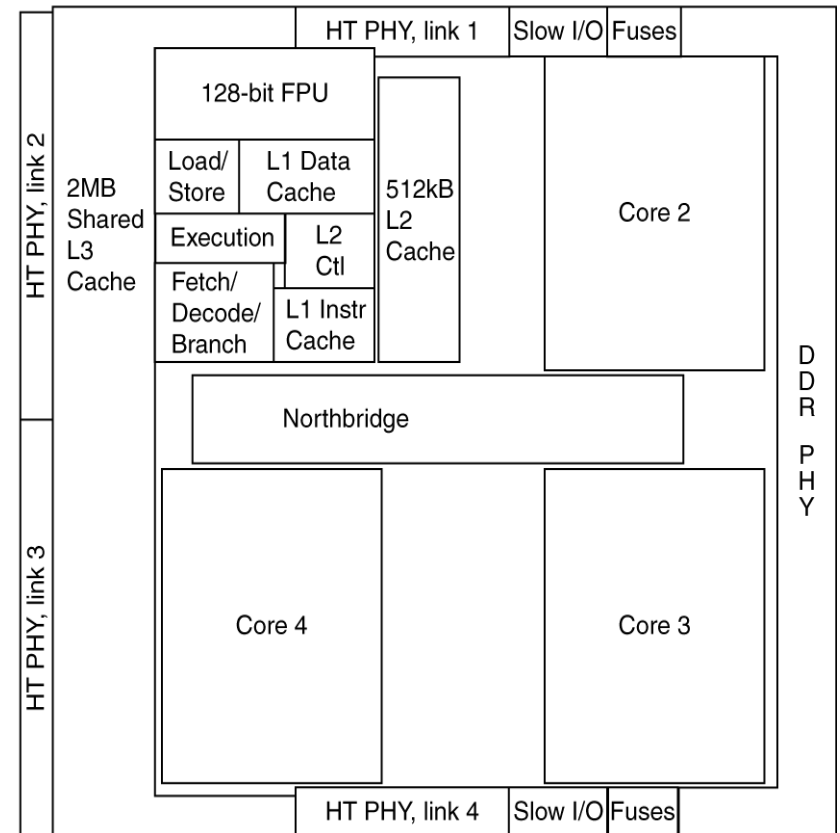 

1. Building a Datapath

❑ **Instruction memory:**


- A memory unit that stores the instructions of a program
- Supplies an instruction given its address

❑ **Program counter:**


- A register storing the address of the instruction being executed

❑ **Adder:**

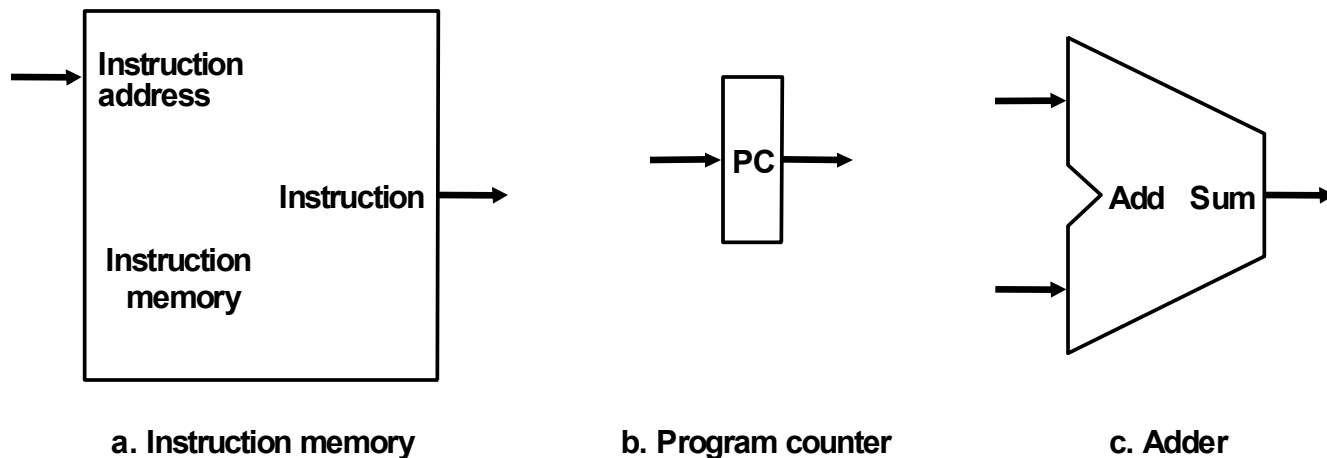- A unit that increments PC to form the address of next instruction



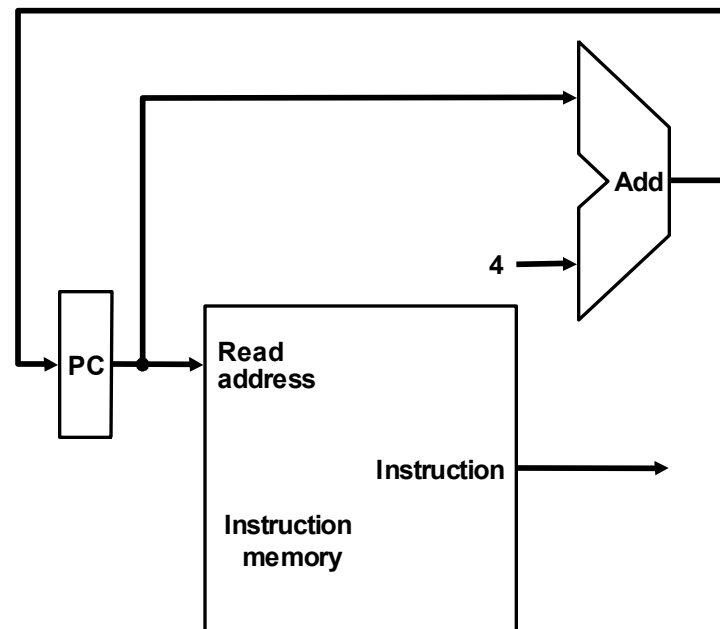
1. Fetch the current instruction from memory using PC
2. Prepare for the next instruction
 - By incrementing PC by 4 to point to next instruction (base case)
 - Will worry about the branches later



□ E.g.: `add $t0, $s1, $s2`

0	17	18	8	0	32
000000	10001	10010	01000	00000	100000
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Register	Value
s1	100
s2	200

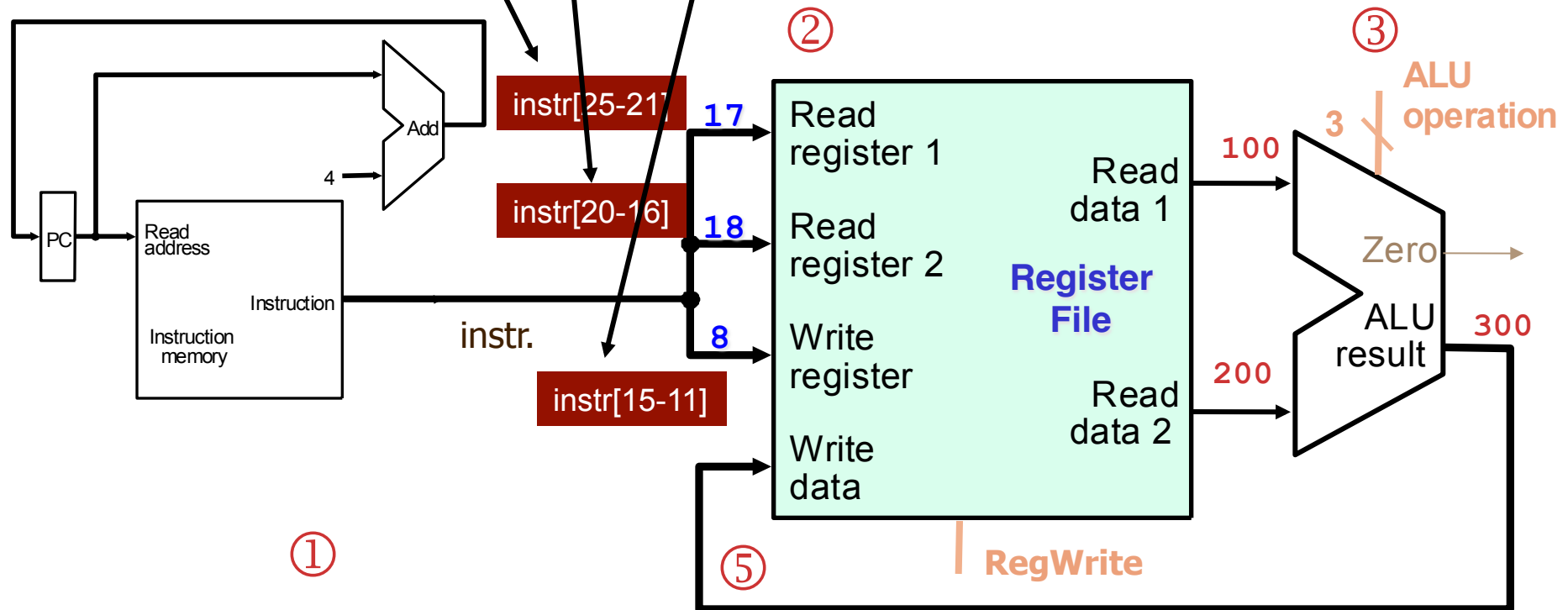

Datapath for Load/Store (I-Format) Instr.


12

□ E.g.: `lw $t0, 1000($s1)`

35	17 (s1)	8 (t0)	1000 (immediate)
100011	10001	01000	0000 0011 1110 1000
6 bits	5 bits	5 bits	16 bits

Register	Value
t0	200
s1	100

Memory[1100]
50

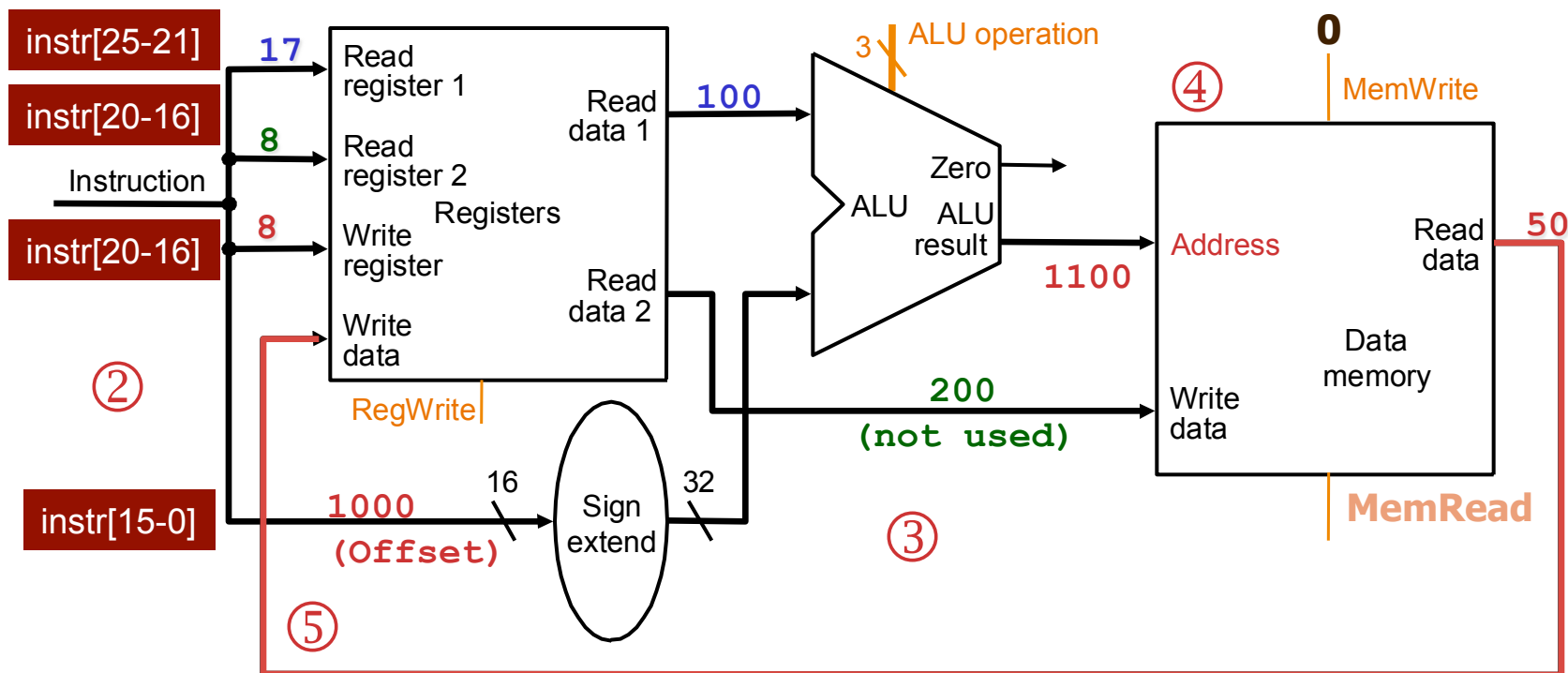


Note: For load word instruction, **MemWrite** has to be de-asserted so that the memory will not be modified by incoming write data.

□ E.g.: `beq $t0, $t1, 2`

```
1000:    beq $t0, $t1, L1
1004:    . 2 instructions
1008:    . are skipped
1012: L1: add $t0, $t1, $t2
```

Register	Value
t0	200
t1	200
PC	1000

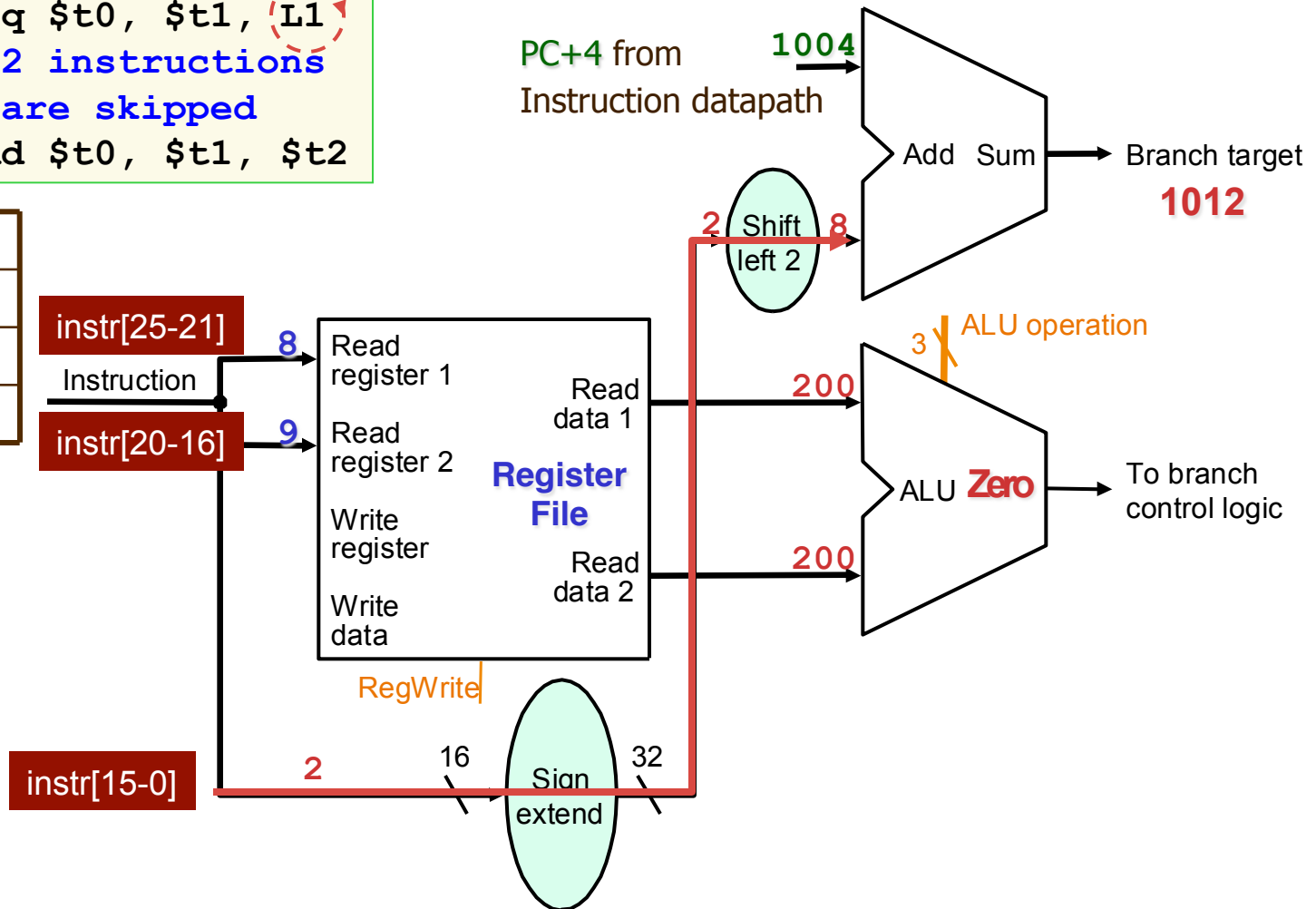


- ❑ We have already built a datapath for each instruction separately
- ❑ Now, we need to combine them into a **single datapath**
- ❑ **Key to combine**


Share some of the resources (e.g., ALU)
among different instructions

Note:

- ❑ This simple implementation is based on the (unrealistic) assumption
 - i.e. all instructions take just one clock cycle each to complete
- ❑ Implication:
 - No datapath resource can be used more than once per instruction
 - Any element needed more than once must be duplicated
 - Instructions and data have to be stored in separate memories

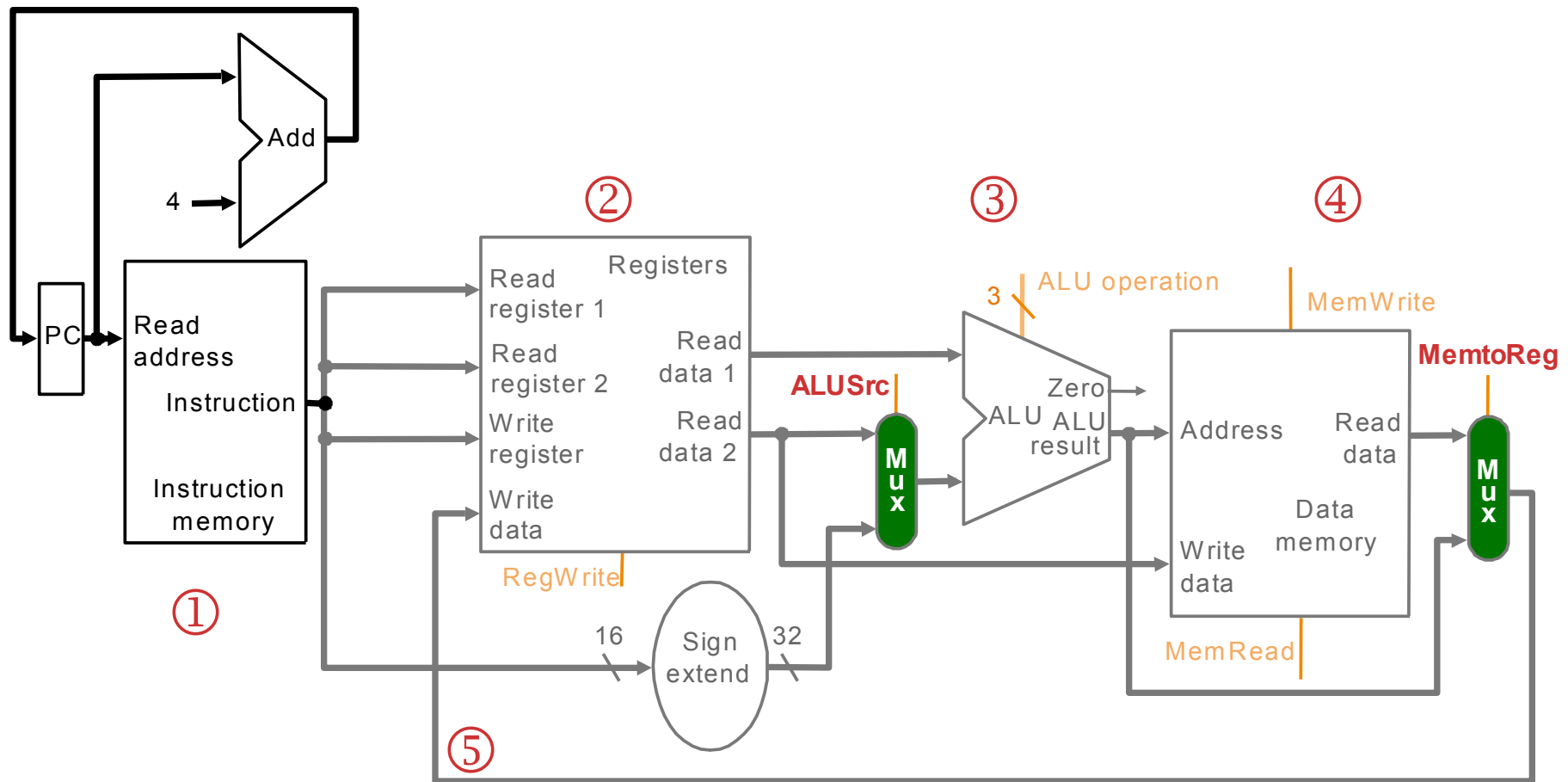- ❑ Use **ALUSrc** to decide which source will be sent to the ALU
- ❑ Use **MemtoReg** to choose the source of output back to dest. register



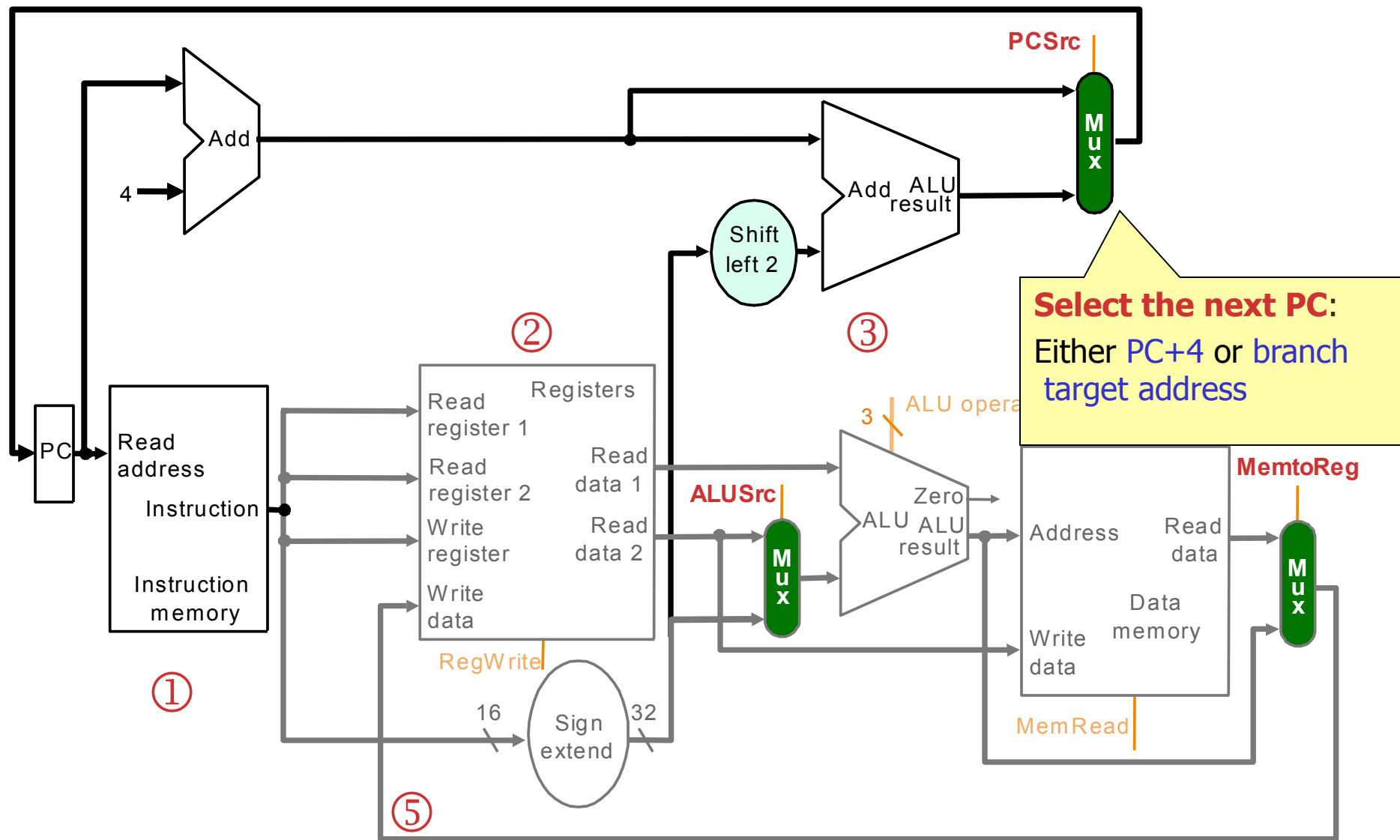

17

