

COMP2611 Spring 2016 Homework #1

(Due Monday Mar 7 5PM)

Note:

- This is an individual assignment; all the work must be your own.
- Submit a pdf file via CASS. Name the pdf file as *<your_stu_id>.pdf* (without the brackets)
- Use Logisim to draw all digital circuits, and paste the image into your homework.

Question 1: Data representation, conversion between bases

- a) Conversion between decimal, binary and hexadecimal. Assume we're dealing with 16 bits signed numbers.

146₍₁₀₎

F0D1₍₁₆₎

- b) Do the same for the same values for 32bits signed numbers.
- c) Do the same for 32 bits unsigned numbers.
- d) Find the IEEE754 single-precision floating-point representation for the following decimal numbers. Briefly show your steps.
- i. 3.75
- ii. -313.3125
- e) What decimal numbers are represented by the following IEEE754 single-precision floating-point representations? Write your answer in decimal (scientific notation is fine). Briefly show your steps.

i. 0 00000000 111000000000000000000000

ii. 1 10000001 000110000000000000000000

Question 2: Boolean algebra and Combinational logic


- a) Simplify the following logic equation using the laws of Boolean algebra only.

$$\overline{ABC + \bar{A}B}$$

- b) Simplify the following logic equation using K-map.

$$\bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C + ABC$$

- c) Given the following logic circuit, give the corresponding logic equation in product of sums form then in sum of products form, and finally, using K-map, simplify this latter. (Note that the prime notation represents inversion)

 

Question 3: Sequential logic

During the lecture, we explained how to build an unlocked SR-latch from a pair of cross-coupled NOR gates. Starting from that circuit show how to:

- Construct an SR-latch with one AND gate, one OR gate, and as many NOT gates as needed, and inputs S and R are active if deasserted (i.e., Set when S=0, Reset when R=0). Write down the truth table and draw your circuit.
- Construct an SR-latch with one AND gate, one OR gate and as many NOT gates as needed, and inputs S and R are active if asserted (that is, Set when S=1, Reset when R=1). Write down the truth table and draw your circuit.

Now consider the following clocked SR-latch built with NAND gates. Draw the output Q versus clock, Set, and Reset inputs, assuming inputs Set and Reset are active in the high state (i.e., when asserted).

